

Inductance

Self-inductance

the induced emf tends to oppose the direction of emf of the battery (Lenz's Law)

Inductor

self-induced emf ε_L

$$\varepsilon_L = -L \frac{dI}{dt}$$


L is inductance of the inductor coil

Inductance of the Inductor

$$\varepsilon_L = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$$

$$\Rightarrow L = \frac{N\Phi_B}{I}$$

RL Circuit Charging

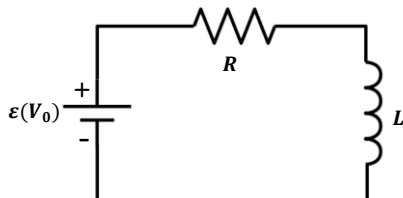

apply Kirchhoff's rule clockwise:

$$\varepsilon - IR - L \frac{dI}{dt} = 0 \Rightarrow IR + L \frac{dI}{dt} = V_0$$

when time $t \rightarrow \infty$, I tends to be a stable value I_∞ , $dI \rightarrow 0$

$$I_\infty = \frac{V_0}{R}$$

assume $I(t) = I_\infty + \tilde{I}(t)$, where $\tilde{I}(t)$ is the difference


$$\Rightarrow L \frac{d\tilde{I}}{dt} + R\tilde{I} + RI_\infty = V_0 \Rightarrow \frac{d\tilde{I}}{dt} = -\frac{R}{L} \tilde{I}$$

$$\Rightarrow \tilde{I} = \tilde{I}_0 e^{-\frac{Rt}{L}}$$

$$\Rightarrow I(t) = \frac{V_0}{R} + \tilde{I}_0 e^{-\frac{Rt}{L}} = \frac{V_0}{R} + \left(-\frac{V_0}{R}\right) e^{-\frac{Rt}{L}}$$

$$\Rightarrow I(t) = \frac{V_0}{R} \left(1 - e^{-\frac{Rt}{L}}\right)$$

RL Circuit Discharging

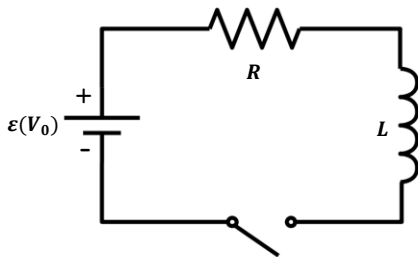

after the current reaches the maximum, remove the switch

$$L \frac{dI}{dt} = IR$$

$$\Rightarrow I(t) = \frac{V_0}{R} e^{-\frac{Rt}{L}}$$

Energy in a Magnetic Field

$$U = \int I^2 R = \int_0^\infty I_0^2 e^{-\frac{2Rt}{L}} R = I_0^2 R \frac{L}{2R} = \frac{1}{2} L I_0^2$$

$$\Rightarrow \boxed{U = \frac{1}{2} L I_0^2}$$